

LC Circuit: Application (2)



At time $t = 0$ a charge $Q = 2C$ is on each capacitor and all currents are zero.

- (a) What is the energy stored in the circuit?
- (b) At what time t_1 are the capacitors discharged for the first time?
- (c) What is the current through each inductor at time t_1 ?

