


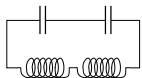
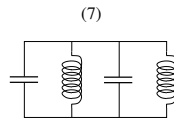
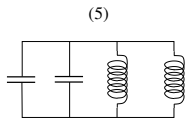


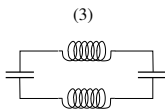

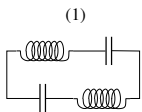
In these LC circuits all capacitors have equal capacitance C and all inductors have equal inductance L . Sort the circuits into groups that are equivalent.




(2)

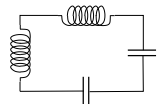

(4)

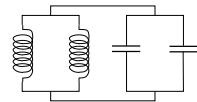

(6)

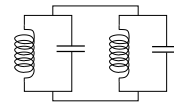

(8)