



In this RLC circuit, we know the voltage amplitudes V_R, V_C, V_L across each device, the current amplitude $I_{max} = 5A$, and the angular frequency $\omega = 2\text{rad/s}$.

- Find the device properties R, C, L and the voltage amplitude \mathcal{E}_{max} of the ac source.

