

AC Circuit Application (4)



Given the current amplitudes I_1, I_2, I_3 through the three branches of this RLC circuit, and given the amplitude $\mathcal{E}_{max} = 100\text{V}$ and angular frequency $\omega = 500\text{rad/s}$ of the ac source, find the device properties R, L, C .

