



Find the current amplitudes I_1, I_2, I_3, I_4 in the four RLC circuits shown.

