



Consider an RLC series circuit with inductance $L = 88\text{mH}$, capacitance $C = 0.94\mu\text{F}$, and unknown resistance R .

The ac generator $\mathcal{E} = \mathcal{E}_{\max} \sin(\omega t)$ has amplitude $\mathcal{E}_{\max} = 24\text{V}$ and frequency $f = 930\text{Hz}$. The phase angle is $\delta = 75^\circ$.

- (a) Find the resistance R .
- (b) Find the current amplitude I_{\max} .
- (c) Find the maximum energy U_L^{\max} stored in the inductor.
- (d) Find the maximum energy U_C^{\max} stored in the capacitor.
- (e) Find the time t_1 at which the current has its maximum value I_{\max} .
- (f) Find the time t_2 at which the charge on the capacitor has its maximum value Q_{\max} .