



Consider the two ac circuits shown.

- (a) In the circuit on the left, determine the current amplitude  $I_1$  and the voltage amplitudes  $V_1$  and  $V_2$ .
- (b) In the circuit on the right, determine the current amplitudes  $I_2$ ,  $I_3$ , and  $I_4$ .

