

## RLC Circuit: Application (3)



In the circuit shown the capacitor is without charge and the switch is in position  $a$ .

(i) When the switch is moved to position  $b$  we have an  $RC$  circuit with the capacitor being charged up gradually:  $Q(t) = \mathcal{E}C[1 - e^{-t/\tau}]$ .

Find the time constant  $\tau$  and the charge  $Q_{max}$  after a long time.

(ii) Then we reset the clock and move the switch from  $b$  to  $c$ .

We now have a an  $LC$  circuit:  $Q(t) = Q_{max} \cos(\omega t)$ .

Find the angular frequency of oscillation  $\omega$  and the maximum current  $I_{max}$  that flows through the inductor periodically.

