
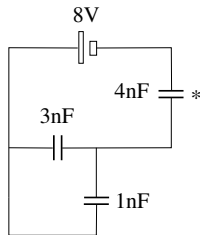


Unit Exam II: Problem #1 (Fall '15)

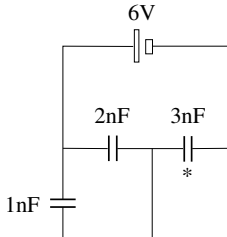



Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF -capacitor.



Unit Exam II: Problem #1 (Fall '15)



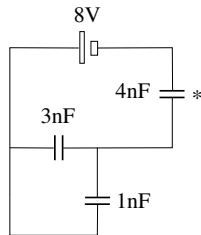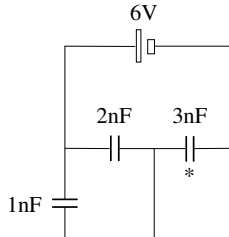Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF-capacitor.





Solution:

$$(a) C_{eq} = \left(\frac{1}{1\text{nF} + 2\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 1.5\text{nF}$$

Unit Exam II: Problem #1 (Fall '15)



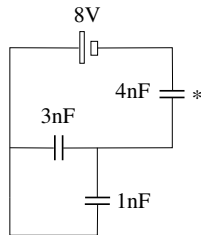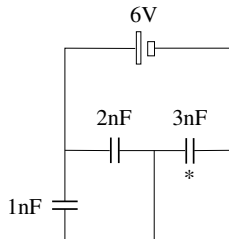Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF-capacitor.



Solution:



$$(a) C_{eq} = \left(\frac{1}{1\text{nF} + 2\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 1.5\text{nF}$$

$$(b) U = \frac{1}{2} (1.5\text{nF})(6\text{V})^2 = 27\text{nJ}$$

Unit Exam II: Problem #1 (Fall '15)



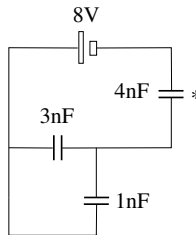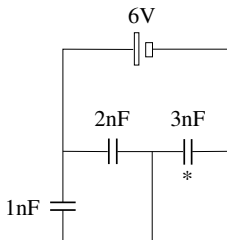Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF-capacitor.



Solution:

$$(a) C_{eq} = \left(\frac{1}{1\text{nF} + 2\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 1.5\text{nF}$$



$$(b) U = \frac{1}{2} (1.5\text{nF}) (6\text{V})^2 = 27\text{nJ}$$

$$(c) V_* = \frac{1}{2} 6\text{V} = 3\text{V}$$

Unit Exam II: Problem #1 (Fall '15)



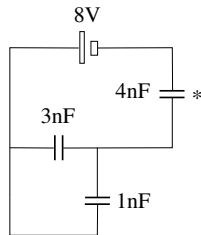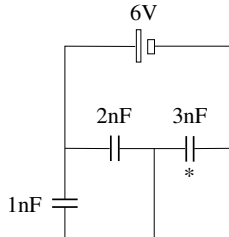Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF-capacitor.



Solution:

$$(a) C_{eq} = \left(\frac{1}{1\text{nF} + 2\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 1.5\text{nF}$$

$$(b) U = \frac{1}{2} (1.5\text{nF}) (6\text{V})^2 = 27\text{nJ}$$



$$(c) V_* = \frac{1}{2} 6\text{V} = 3\text{V}$$

$$(d) V_1 = 6\text{V} - 3\text{V} = 3\text{V}$$

Unit Exam II: Problem #1 (Fall '15)



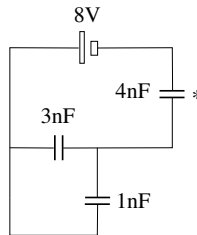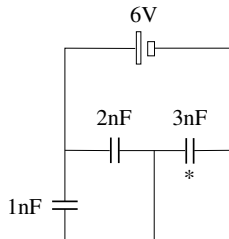Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF-capacitor.



Solution:

$$(a) C_{eq} = \left(\frac{1}{1\text{nF} + 2\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 1.5\text{nF}$$

$$(b) U = \frac{1}{2} (1.5\text{nF}) (6\text{V})^2 = 27\text{nJ}$$

$$(c) V_* = \frac{1}{2} 6\text{V} = 3\text{V}$$



$$(d) V_1 = 6\text{V} - 3\text{V} = 3\text{V}$$

$$(a) C_{eq} = \left(\frac{1}{3\text{nF} + 1\text{nF}} + \frac{1}{4\text{nF}} \right)^{-1} = 2\text{nF}$$

Unit Exam II: Problem #1 (Fall '15)



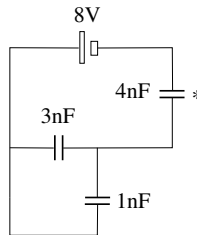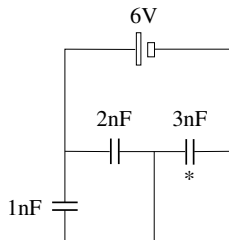Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF-capacitor.



Solution:

$$(a) C_{eq} = \left(\frac{1}{1\text{nF} + 2\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 1.5\text{nF}$$

$$(b) U = \frac{1}{2} (1.5\text{nF})(6\text{V})^2 = 27\text{nJ}$$

$$(c) V_* = \frac{1}{2} 6\text{V} = 3\text{V}$$

$$(d) V_1 = 6\text{V} - 3\text{V} = 3\text{V}$$



$$(a) C_{eq} = \left(\frac{1}{3\text{nF} + 1\text{nF}} + \frac{1}{4\text{nF}} \right)^{-1} = 2\text{nF}$$

$$(b) U = \frac{1}{2} (2\text{nF})(8\text{V})^2 = 64\text{nJ}$$

Unit Exam II: Problem #1 (Fall '15)



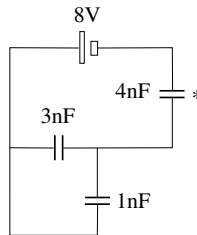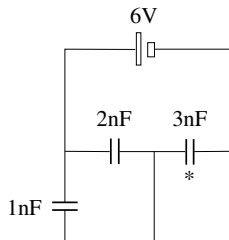Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF-capacitor.



Solution:

$$(a) C_{eq} = \left(\frac{1}{1\text{nF} + 2\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 1.5\text{nF}$$

$$(b) U = \frac{1}{2} (1.5\text{nF})(6\text{V})^2 = 27\text{nJ}$$

$$(c) V_* = \frac{1}{2} 6\text{V} = 3\text{V}$$

$$(d) V_1 = 6\text{V} - 3\text{V} = 3\text{V}$$

$$(a) C_{eq} = \left(\frac{1}{3\text{nF} + 1\text{nF}} + \frac{1}{4\text{nF}} \right)^{-1} = 2\text{nF}$$



$$(b) U = \frac{1}{2} (2\text{nF})(8\text{V})^2 = 64\text{nJ}$$

$$(c) V_* = \frac{1}{2} 8\text{V} = 4\text{V}$$

Unit Exam II: Problem #1 (Fall '15)



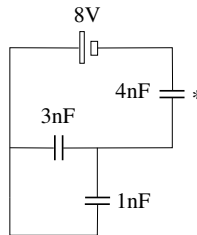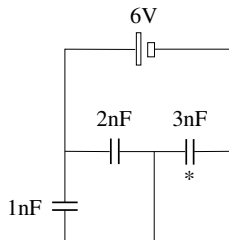Consider the capacitor circuit shown at equilibrium. (a) Find the equivalent capacitance C_{eq} . (b) Find the total energy U stored in the three capacitors. (c) Find the voltage V_* across the capacitor marked by an asterisk. (d) Find the voltage V_1 across the 1nF-capacitor.



Solution:

$$(a) C_{eq} = \left(\frac{1}{1\text{nF} + 2\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 1.5\text{nF}$$

$$(b) U = \frac{1}{2} (1.5\text{nF})(6\text{V})^2 = 27\text{nJ}$$

$$(c) V_* = \frac{1}{2} 6\text{V} = 3\text{V}$$

$$(d) V_1 = 6\text{V} - 3\text{V} = 3\text{V}$$

$$(a) C_{eq} = \left(\frac{1}{3\text{nF} + 1\text{nF}} + \frac{1}{4\text{nF}} \right)^{-1} = 2\text{nF}$$

$$(b) U = \frac{1}{2} (2\text{nF})(8\text{V})^2 = 64\text{nJ}$$

$$(c) V_* = \frac{1}{2} 8\text{V} = 4\text{V}$$

$$(d) V_1 = 8\text{V} - 4\text{V} = 4\text{V}$$